

Homework 2

Rhea Mae Edwards
Student ID #
932-389-303

- 1) Truth Tables, Boolean Logic, Canonical Form, Logic Minimizations, and NAND/NOR Implementation

2.1 Boolean Equations in Sum-of-Products Canonical Form

A	B	Y
0	0	1
0	1	0
1	0	1
1	1	1

$$y(A, B) = \Sigma(0, 2, 3)$$

$$y = A'B' + AB' + AB$$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$$y(A, B, C) = \Sigma(0, 7)$$

$$y = A'B'C' + ABC$$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$$y(A, B, C) = \Sigma(0, 2, 4, 5, 7)$$

$$y = A'B'C' + A'BC' + AB'C' + ABC + ABC$$

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

$$y(A, B, C, D) = \Sigma(0, 1, 2, 3, 8, 10, 14)$$

$$y = A'B'C'D' + A'B'C'D + A'B'CD' + A'B'CD + AB'C'D' + AB'CD' + ABCD'$$

e)	A	B	C	D	y
	0	0	0	0	1
	0	0	0	1	0
	0	0	1	0	0
	0	0	1	1	1
	0	1	0	0	0
	0	1	0	1	0
	0	1	1	0	0
	0	1	1	1	1
	1	0	0	0	0
	1	0	0	1	0
	1	0	1	0	0
	1	0	1	1	1
	1	1	0	0	0
	1	1	0	1	0
	1	1	1	0	1
	1	1	1	1	1

$$y(A, B, C, D) = \sum(0, 3, 5, 6, 9, 10, 12, 15)$$

$$\boxed{Y = A'B'C'D' + A'B'CD + A'BC'D + A'BCD' + ABC'D + AB'C'D' + ABC'D' + ABCD}$$

22 Boolean Equations in Sum-of-Products Canonical Form

a)	A	B	y
	0	0	0
	0	1	1
	1	0	1

$$y(A, B) = \sum(1, 2, 3)$$

$$\boxed{Y = A'B + AB' + AB}$$

b)	A	B	C	y
	0	0	0	0
	0	0	1	1
	0	1	0	1
	0	1	1	1
	1	0	0	0
	1	0	1	0
	1	1	0	1
	1	1	1	0

$$y(A, B, C) = \sum(1, 2, 3, 4, 6)$$

$$\boxed{Y = A'B'C + ABC' + A'BC + AB'C' + ABC'}$$

c)	A	B	C	y
	0	0	0	0
	0	0	1	1
	0	1	0	0
	0	1	1	0
	1	0	0	0
	1	0	1	0
	1	1	0	1
	1	1	1	1

$$y(A, B, C) = \sum(1, 6, 7)$$

$$\boxed{Y = A'B'C + ABC' + ABC}$$

23 Boolean Equations in Product-of-Sums Canonical Form

a)

A	B	Y
0	0	1
0	1	0
1	0	1

$$Y(A, B) = \pi(1)$$

$$Y = A + B'$$

b)

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$Y(A, B, C) = \pi(1, 2, 3, 4, 5, 6)$$

$$Y = (A + B + C') + (A + B' + C) + (A + B' + C') + \\ (A' + B + C) + (A' + B + C') + (A' + B' + C)$$

c)


A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$Y(A, B, C) = \pi(1, 3, 6)$$

$$Y = (A + B + C') + (A + B' + C') + (A' + B' + C)$$


25 Minimize Boolean equations from Exercise 21

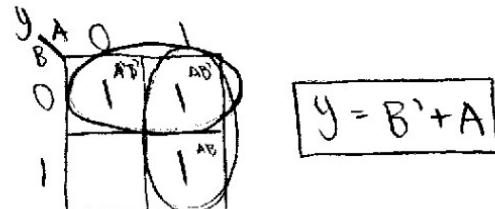a) $Y = A'B' + AB' + AB$
 $Y(A, B) = \Sigma(0, 2, 3)$




$$Y = B' + A$$

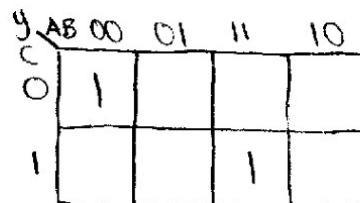b) $Y = A'B'C' + ABC$
 $Y(A, B, C) = (0, 7)$



$$Y = A'B'C' + ABC$$

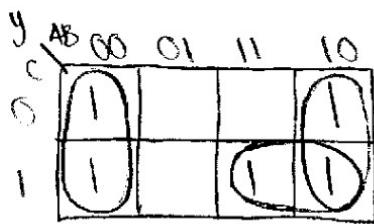
c) $Y = A'BC + A'BC' + AB'C + ABC' + ABC$
 $Y(A, B, C) = (0, 2, 4, 5, 7)$



$$Y = A'B' + AC + AB'$$

2.6 Minimize Boolean Equations from Exercise 2.2

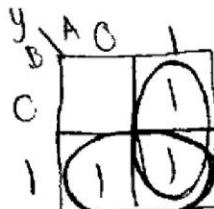
a) $y(A, B) = \sum(1, 2, 3)$
 $y = A'B + AB' + AB$




$$y = A + B$$

b) $y(A, B, C) = \sum(1, 2, 3, 4, 6)$
 $y = A'B'C + A'BC' + A'BC + ABC' + ABC$

$$y = AC + A'C + A'B$$

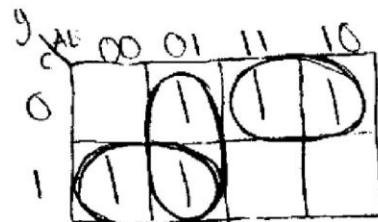

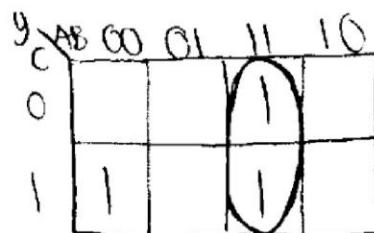
c) $y(A, B, C) = \sum(1, 6, 7)$
 $y = A'B'C + ABC' + ABC$



$$y = AB + A'B'C$$

2.28 Minimal Boolean Equation

A	B	C	D	y
0	0	0	0	X
0	0	0	1	X
0	0	1	0	X
0	0	1	1	0
0	1	0	0	0
0	1	0	1	X
0	1	1	0	X
0	1	1	1	0
1	0	0	0	X
1	0	0	1	1
1	0	1	0	1
1	0	1	1	X
1	1	0	0	1
1	1	0	1	1
1	1	1	0	X
1	1	1	1	1

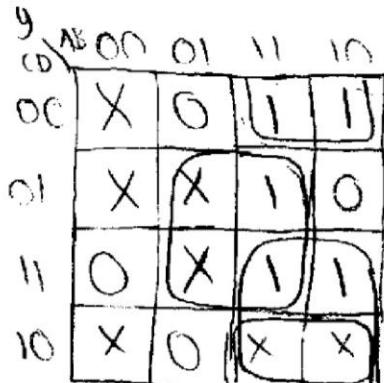

$$y = AC + BD + AD$$

2) Spring Picnics

2.33 Ben Bittiddle is Picky about his Picnics

E = enjoyment

S = Sun

A = ants

H = hummingbirds

L = ladybugs

$$E(S, A, H, L) = \Sigma(2, 3, 5, 6, 7, 8, 9, 10, 11, 13, 14, 15)$$

$$E(S, A, H, L) = \Pi(0, 1, 4, 12)$$

S	A	H	L	E
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Just based off the description given by the problem statement we can conclude that...

$$E = SA' + H + AL$$

3) Combinational Logic Design

2.34 Design of a Seven-Segment Decoder

A	B	C	D	SegA
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


$$\text{SegA}(A, B, C, D) = \Sigma(1, 4)$$

		AB	CD	00	01	11	10
		00					
00	01	00		1			
		01					
01	10	00					
		01					
10	11	00					
		01					
11	10	00					
		01					

$$\text{SegA} = \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}\bar{D}$$

A	B	C	D	SegB
0	0	0	0	00000000
0	0	0	1	00000000
0	0	1	0	00000000
0	0	1	1	00000000
0	1	0	0	00000000
0	1	0	1	00000000
0	1	1	0	00000000
0	1	1	1	00000000
1	0	0	0	00000000
1	0	0	1	00000000
1	0	1	0	00000000
1	0	1	1	00000000
1	1	0	0	00000000
1	1	0	1	00000000
1	1	1	0	00000000
1	1	1	1	00000000

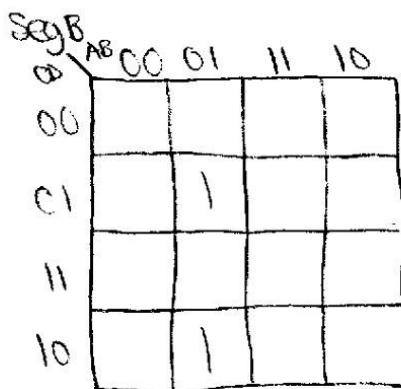
$$\text{segB}(A, B, C, D) = \Sigma(5, 6)$$



$$\text{segA} = \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D}$$

A	B	C	D	SegC
0	0	0	0	00000000
0	0	0	1	00000000
0	0	1	0	00000000
0	0	1	1	00000000
0	1	0	0	00000000
0	1	0	1	00000000
0	1	1	0	00000000
0	1	1	1	00000000
1	0	0	0	00000000
1	0	0	1	00000000
1	0	1	0	00000000
1	0	1	1	00000000
1	1	0	0	00000000
1	1	0	1	00000000
1	1	1	0	00000000
1	1	1	1	00000000


$$\text{segC}(A, B, C, D) = \Sigma(2)$$

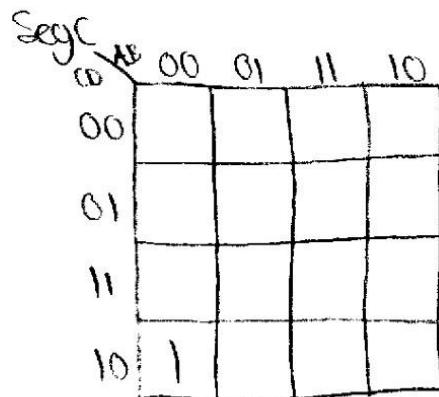

$$\text{segC} = \bar{A}\bar{B}\bar{C}\bar{D}$$

A	B	C	D	SegD
0	0	0	0	00000000
0	0	0	1	00000000
0	0	1	0	00000000
0	0	1	1	00000000
0	1	0	0	00000000
0	1	0	1	00000000
0	1	1	0	00000000
0	1	1	1	00000000
1	0	0	0	00000000
1	0	0	1	00000000
1	0	1	0	00000000
1	0	1	1	00000000
1	1	0	0	00000000
1	1	0	1	00000000
1	1	1	0	00000000
1	1	1	1	00000000


A	B	C	D	SegD
1	1	0	1	0
1	1	1	0	0

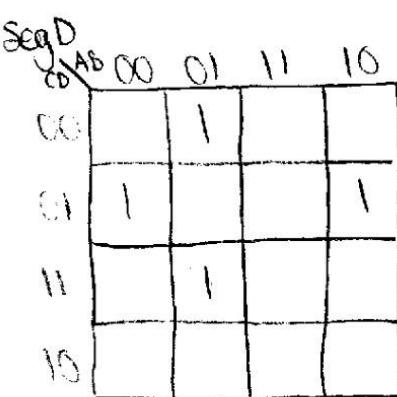

$$\text{segD} = \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D}$$

A	B	C	D	Seg E
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

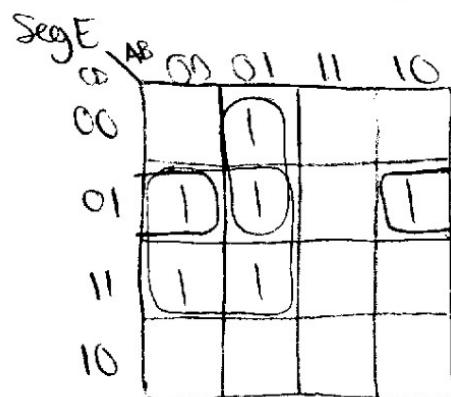
$$\text{SegE}(A, B, C, D) = \sum(1, 3, 4, 5, 7, 9)$$



$$\text{SegE} = \overline{AD} + \overline{ABC} + \overline{BC}D$$

A	B	C	D	Seg F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0
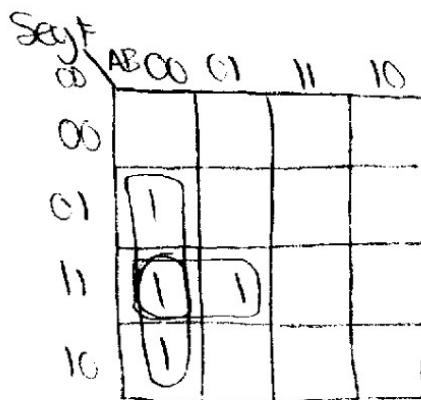
$$\text{SegF}(A, B, C, D) = \sum(1, 2, 3, 7)$$



$$\text{SegF} = \overline{ACD} + \overline{A}\overline{B}D + \overline{A}\overline{B}C$$


A	B	C	D	Seg G
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

$$\text{SegG}(A, B, C, D) =$$

$$\sum(0, 1, 7)$$

$$\text{SegG} = \overline{ABC} + \overline{AB}CD$$

A	B	C	D	Seg G
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0
1	0	1	0	0
1	0	1	1	1
1	0	0	0	0
1	0	0	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
0	0	1	0	0
0	0	1	1	1
0	0	0	0	0
0	0	0	1	0

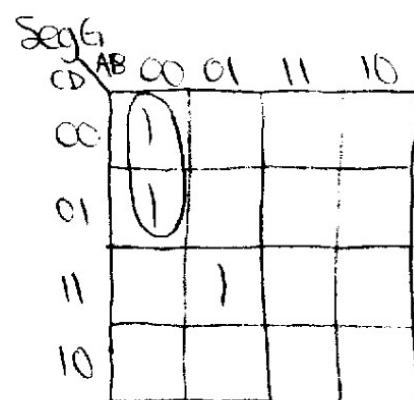

A	B	C	D	SegA
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	X
1	0	0	1	X
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

$$\text{SegA}(A, B, C, D) = \Sigma(1, 4)$$

SegA

CD	AB	00	01	11	10
00		(1)	X		
01		1		X	
11				X	X
10				X	X

$$\text{SegA} = B\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D}$$

A	B	C	D	SegB
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	X
1	0	0	1	X
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

$$\text{SegB}(A, B, C, D) = \Sigma(5, 6)$$

SegB

CD	AB	00	01	11	10
00			X		
01		(1)	X		
11			X	X	
10		(1)	X		X

$$\text{SegB} = B\bar{C}D + BC\bar{D}$$

A	B	C	D	SegC
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	X
1	0	0	1	X
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

$$\text{SegC}(A, B, C, D) =$$

$$\Sigma(2)$$

$$\text{SegC} = \bar{B}C\bar{D}$$

SegC

CD	AB	00	C1	11	10
00				X	
01				X	
11				X	X
10		(1)		X	X

A	B	C	D	SegD
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	x
1	1	1	0	x
1	1	1	1	x

$$\text{SegD}(A, B, C, D) = \Sigma(1, 4, 7, 9)$$

SegD

AB	00	01	11	10
CD	00	(1) X		
00	1	X	1	
01		(1) X		
11		(1) X	X	
10			X	X

$$\text{SegD} = \overline{B}\overline{C}D + B\overline{C}\bar{D} + BCD$$

A	B	C	D	SegE
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	x
1	1	1	0	x
1	1	1	1	x

$$\text{SegE}(A, B, C, D) = \Sigma(1, 3, 4, 5, 7, 9)$$

SegE

AB	00	01	11	10
CD	00	(1) X		
00	1	(1) X	1	
01		1	X	1
11		1	X	X
10			X	X

$$\text{SegE} = D + B\overline{C}$$

A	B	C	D	SegF
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	x
1	1	1	0	x
1	1	1	1	x

A	B	C	D	SegF
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

$$\begin{aligned} \text{SegF}(A, B, C, D) = \\ \Sigma(1, 2, 3, 7) \end{aligned}$$

SegF

AB	00	01	11	10
CD	00			X
00	1		X	
01		1	X	
11		1	1	X
10	1		X	X

$$\text{SegF} = CD + \overline{B}C + \overline{A}\overline{B}D$$


A	B	C	D	Seg6
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	X
1	0	0	1	X
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

$$\text{SegG}(A, B, C, D) = \Sigma(0, 1, 7)$$

SegG	AB	00	01	11	10
CD	00	1 1	X		
00			X		
01				X	
11			(1 X) X		
10				X X	

$$\text{SegG} = \bar{A}\bar{B}\bar{C} + BCD$$


c)

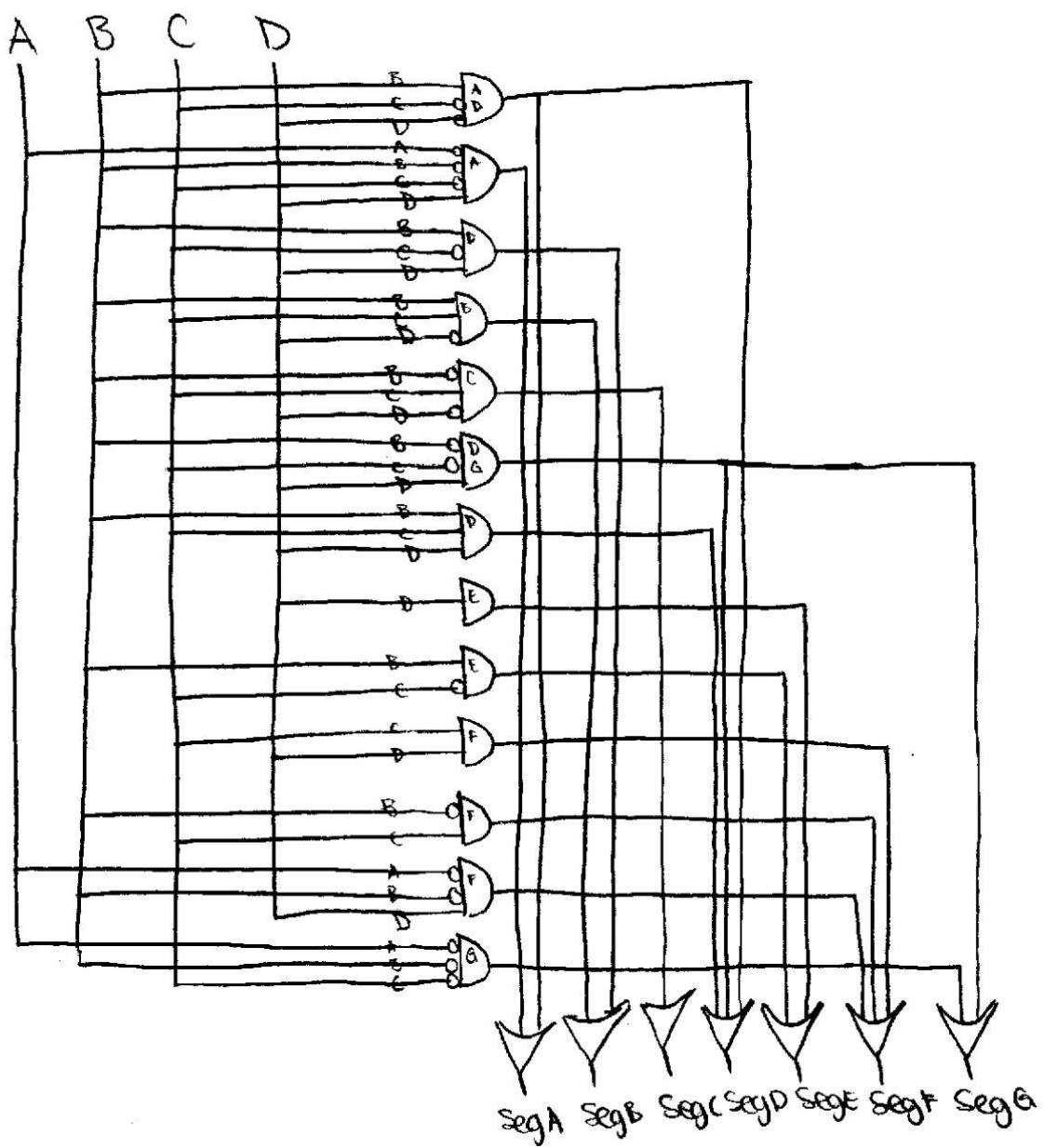


2.35 Boolean Equation and Sketch of a 4-Input and 2-Output Circuit

A	B	C	D	P	D
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	0	1	0	0
0	1	1	0	0	1
0	1	1	1	1	0
1	0	0	0	0	0
1	0	0	1	0	1
1	0	1	0	0	0
1	0	1	1	0	1
1	1	0	0	0	0
1	1	0	1	0	0
1	1	1	0	0	1
1	1	1	1	1	1
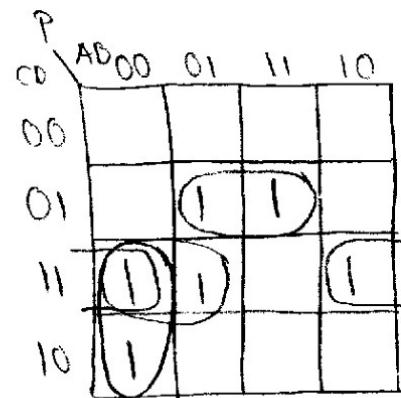
$$P(A, B, C, D) = \sum(2, 3, 5, 7, 11, 13)$$


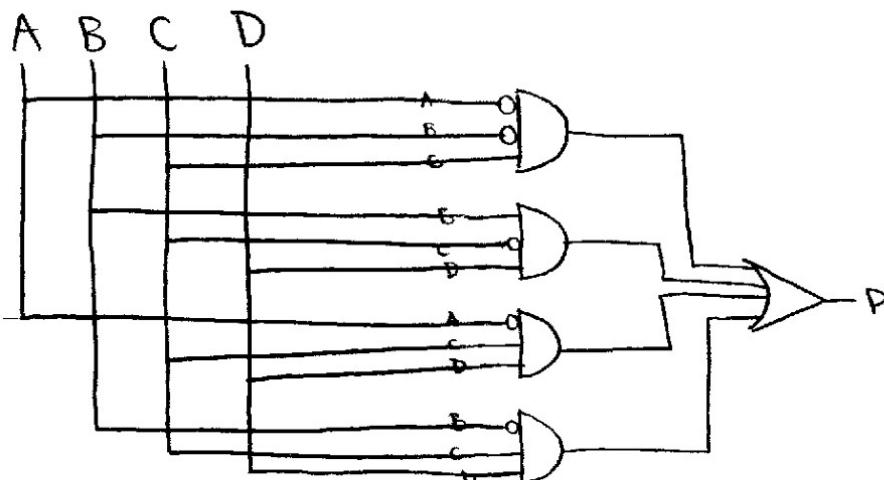
$$P = \bar{A}\bar{B}C + B\bar{C}D + \bar{A}C\bar{D} + \bar{B}CD$$



4) Timing

2.43 Propagation Delay and Contamination Delay of Figure 2.83

$$\begin{aligned} t_{PD} &= \text{One 2-Input NAND Gate} + \text{One 2-Input NAND Gate} + \\ &\quad \text{One 2-Input NAND Gate} = \\ &\quad 3(\text{2-Input NAND Gate}) = 3(20) = 60 \text{ ps} \end{aligned}$$

$$\begin{aligned} t_{CD} &= \text{One 2-Input NAND Gate} = \\ &\quad 1(\text{2-Input NAND Gate}) = 1(15) = 15 \text{ ps} \end{aligned}$$

$$t_{PD} = 60 \text{ ps}$$

$$t_{CD} = 15 \text{ ps}$$

2.44 Propagation Delay and Contamination Delay of Figure 2.84

$$t_{PD} = \text{One 2-Input AND Gate} + \text{One 2-Input NOR Gate} + \\ \text{One 2-Input NOR Gate} + \text{One NOT Gate} = \\ 1(\text{2-Input AND Gate}) + 2(\text{2-Input NOR Gate}) + \\ 1(\text{NOT Gate}) = 1(30) + 2(30) + 1(15) = 105 \text{ ps}$$

$$t_{CD} = \text{One 2-Input NAND Gate} + \text{One 2-Input NOR Gate} + \\ \text{One NOT Gate} = \\ 1(\text{2-Input NAND Gate}) + 1(\text{2-Input NOR Gate}) + \\ 1(\text{NOT Gate}) = 1(15) + 1(25) + 1(10) = 50 \text{ ps}$$

$$\boxed{t_{PD} = 105 \text{ ps}} \\ t_{CD} = 50 \text{ ps}$$

5) Interview Questions

2.3 Tristate Buffer

A tristate buffer with two inputs (a data input and a control input) with an output. It allows the user to control when current passes through the device being used. A tristate buffer is a good way to control what gets on a bus of a device and what doesn't.